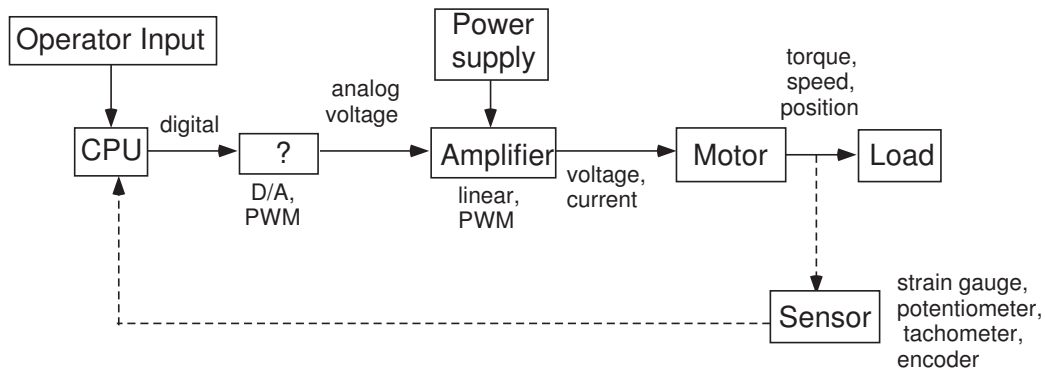


# Motor Control

- Suppose we wish to use a microprocessor to control a motor
  - (or to control the load attached to the motor!)




- Convert discrete signal to analog voltage
  - D/A converter
  - pulse width modulation (PWM)
- Amplify the analog signal
  - power supply
  - amplifier
- Types of power amplifiers
  - linear vs. PWM
  - voltage-voltage vs. transconductance (voltage-current)
- DC Motor
  - How does it work?
- What to control?
  - electrical signals: voltage, current
  - mechanical signals: torque, speed, position
- Sensors: Can we measure the signal we wish to control (feedback control)?

# Outline

- Review of Motor Principles
  - torque vs. speed
  - voltage vs current control
  - with and without load
- D/A conversion vs. PWM generation
  - harmonics
  - advantages and disadvantages
  - creating PWM signals
- power amplifiers
  - linear vs PWM
  - voltage vs transconductance
- Control
  - choice of signal to control
  - open loop
  - feedback
- References are [5], [3], [1], [4], [8], [7], [6], [9]

# Motor Review


- Recall circuit model of motor:

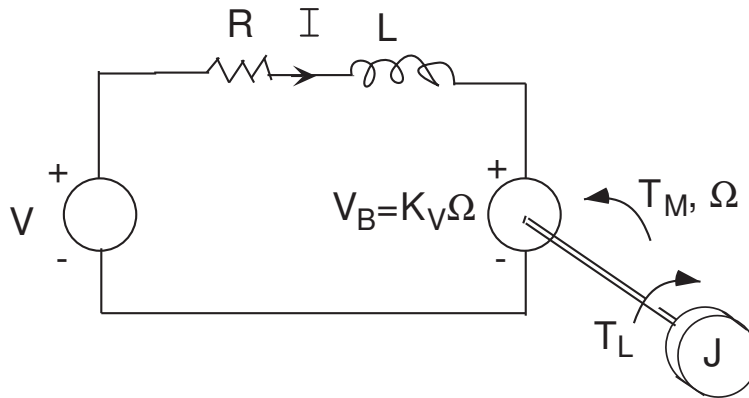

- Suppose motor is driven by a constant voltage source. Then steady state speed and torque satisfy

$$\Omega = \frac{K_M V - R T_L}{K_M K_V + R B}$$
$$T_M = \frac{K_M (V B + K_V T_L)}{K_M K_V + R B}$$

- Torque-speed curve

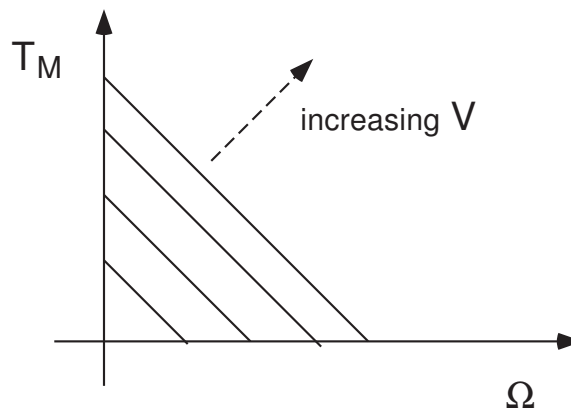

# Voltage Control

- Suppose we attempt to control speed by driving motor with a constant voltage.

- With no load and no friction ( $T_L = 0, B = 0$ )

$$\Omega = \frac{V}{K_V}$$

$$T_M = 0$$

- Recall that torque is proportional to current:  $T_M = K_M I$ . Hence, with no load and no friction,  $I = 0$ , and motor draws no current in steady state.

- Current satisfies

$$I = \frac{V - V_B}{R}$$

- In steady state, back EMF balances applied voltage, and thus current and motor torque are zero.
- With a load or friction, ( $T_L \neq 0$  and/or  $B \neq 0$ )


$$\Omega < \frac{V}{K_V}$$

$$T_M > 0$$


- Speed and torque depend on load and friction
  - friction always present (given in part by motor spec, but there will be additional unknown friction)
  - load torque may also be unknown, or imprecisely known
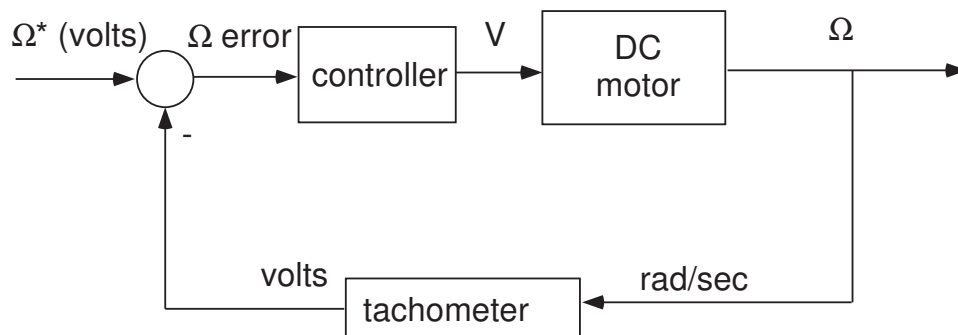
## Issue: Open Loop vs Feedback Control

- Using constant voltage control we cannot specify desired torque or speed precisely due to friction and load
  - an *open loop* control strategy
  - can be resolved by adding a sensor and applying *closed loop*, or *feedback* control
- add a tachometer for speed control



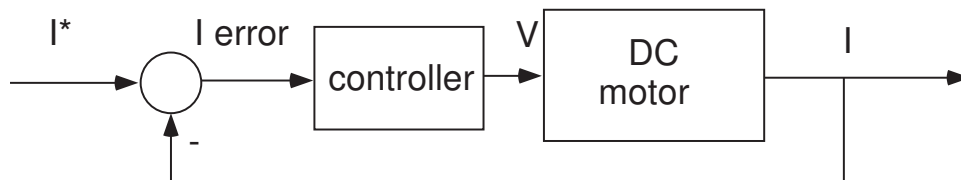- add a current sensor for torque ( $T_M = K_M I$ ) control




- Will study feedback control in Lecture 7.

## Issue: Steady State vs. Transient Response


- Steady state response: the response of the motor to a constant voltage input eventually settles to a constant value
  - the torque-speed curves give steady-state information
- Transient response: the preliminary response before steady state is achieved.
- The transient response is important because
  - transient values of current, voltage, speed, . . . may become too large
  - transient response also important when studying response to nonconstant inputs (sine waves, PWM signals)
- The appropriate tool for studying transient response of the DC motor (or any system) is the *transfer function* of the system
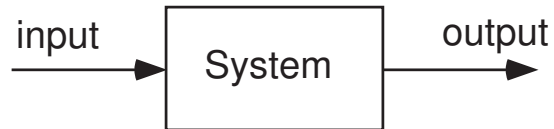
# System

- A *system* is any object that has one or more inputs and outputs




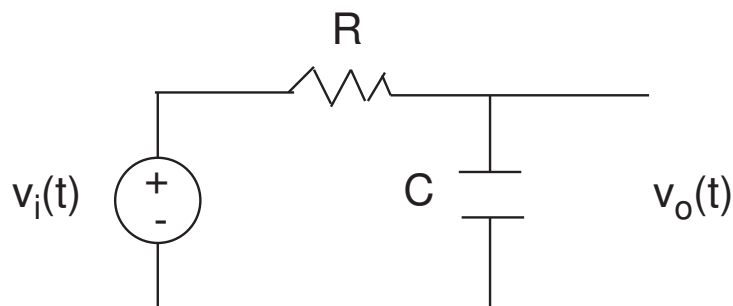- Input: applied voltage, current, foot on gas pedal, . . .
- Output: other variable that responds to the input, e.g., voltage, current, speed, torque, . . .
- Examples:
  - RC circuit



Input: applied voltage, Output: voltage across capacitor

- DC motor

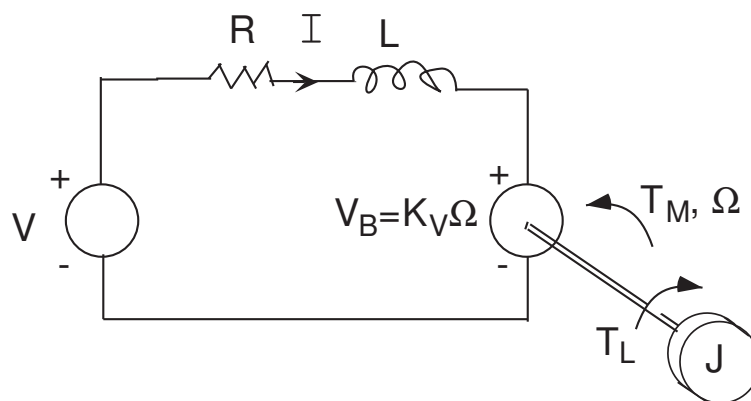

Input: applied voltage, Output: current, torque, speed

# Stability

- We say that a system is *stable* if a bounded input yields a bounded output
- If not, the system is *unstable*
- Consider DC Motor with no retarding torque or friction
  - With constant voltage input, the steady state shaft speed  $\Omega$  is constant  $\Rightarrow$  the system from  $V$  to  $\Omega$  is stable
  - Suppose that we could hold current constant, so that the steady state torque is constant. Since

$$\frac{d\Omega}{dt} = \frac{T_M}{J},$$


the shaft velocity  $\Omega \rightarrow \infty$  and velocity increases without bound  $\Rightarrow$  the system from  $I$  to  $\Omega$  is unstable

- Tests for stability
  - mathematics beyond scope of class
  - we will point out in examples how stability depends on system parameters


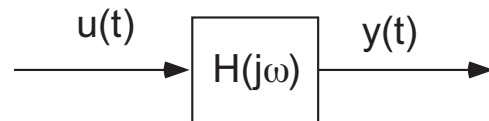
# Frequency Response

- A linear system has a *frequency response* function that governs its response to inputs:



- If the system is *stable*, then the steady state response to a sinusoidal input,  $u(t) = \sin(\omega t)$ , is given by  $H(j\omega)$ :


$$y(t) \rightarrow |H(j\omega)| \sin(\omega t + \angle H(j\omega))$$

- We have seen this idea in Lecture 2 when we discussed anti-aliasing filters and RC circuits
- The response to a constant, or step, input,  $u(t) = u_0, t \geq 0$ , is given by the DC value of the frequency response:


$$y(t) \rightarrow H(0)u_0$$
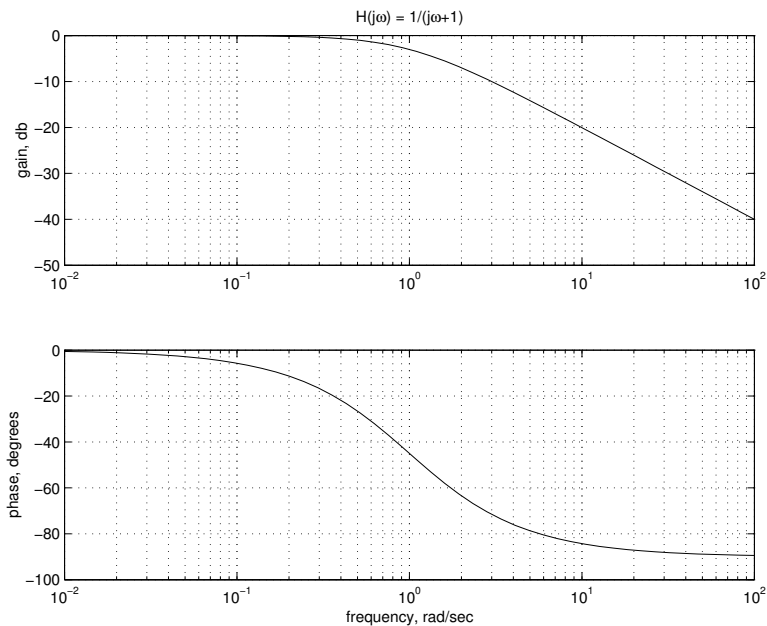
# Bode Plot Example

Lowpass filter<sup>1</sup>,  $H(j\omega) = 1/(j\omega + 1)$



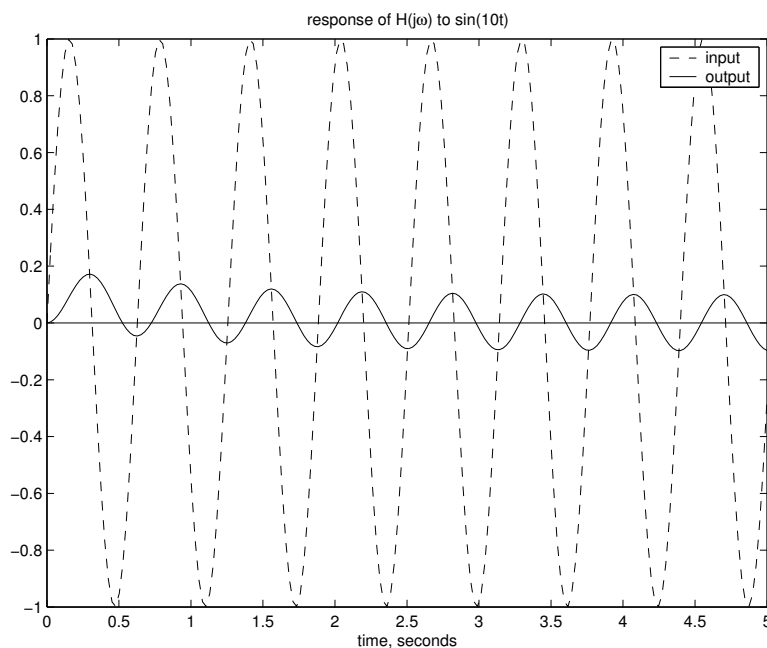Steady state response to input  $\sin(10t)$  satisfies  $y_{ss}(t) = 0.1 \sin(10t - 85^\circ)$ .



<sup>1</sup>MATLAB file bode\_plot.m

# Frequency Response and the Transfer Function

- To compute the frequency response of a system in MATLAB, we must use the *transfer function* of the system.
- (under appropriate conditions) a time signal  $v(t)$  has a Laplace transform

$$V(s) = \int_0^{\infty} v(t)e^{-st} dt$$

- Suppose we have a system with input  $u(t)$  and output  $y(t)$




- The transfer function relates the Laplace transform of the system output to that of its input:

$$Y(s) = H(s)U(s)$$

- for simple systems  $H(s)$  may be computed from the differential equation describing the system
- for more complicated systems,  $H(s)$  may be computed from rules for combining transfer functions
- To find the frequency response of the system, set  $s = j\omega$ , and obtain  $H(j\omega)$
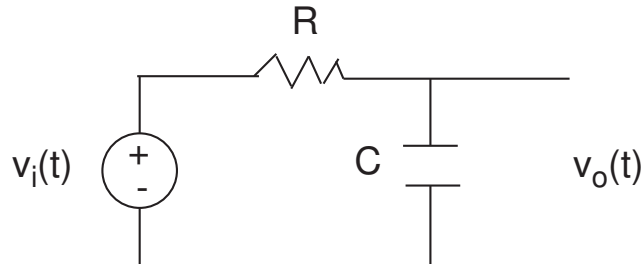
# Transfer Function of an RC Circuit

- RC circuit
  - Input: applied voltage,  $v_i(t)$ .
  - Output: voltage across capacitor,  $v_o(t)$



- differential equation for circuit
  - Kirchoff's Laws:  $v_i(t) - I(t)R = v_o(t)$
  - current/voltage relation for capacitor:  $I(t) = C \frac{dv_o(t)}{dt}$
  - combining yields

$$RC \frac{dv_o(t)}{dt} + v_o(t) = v_i(t)$$

- To obtain transfer function, replace
  - each time signal by its Laplace transform:  $v(t) \rightarrow V(s)$
  - each derivative by "s" times its transform:  $\frac{dv(t)}{dt} \rightarrow sV(s)$
  - solve for  $V_o(s)$  in terms of  $V_i(s)$ :

$$V_o(s) = H(s)V_i(s), \quad H(s) = \frac{1}{RCs + 1}$$

- To obtain frequency response, replace  $j\omega \rightarrow s$

$$H(j\omega) = \frac{1}{RCj\omega + 1}$$

# Transfer Functions and Differential Equations

- Suppose that the input and output of a system are related by a differential equation:

$$\frac{d^n y}{dt^n} + a_1 \frac{d^{n-1} y}{dt^{n-1}} + a_2 \frac{d^{n-2} y}{dt^{n-2}} + \dots + a_{n-1} \frac{dy}{dt} + a_n y =$$
$$b_1 \frac{d^{n-1} u}{dt^{n-1}} + b_2 \frac{d^{n-2} u}{dt^{n-2}} + \dots + b_{n-1} \frac{du}{dt} + b_n u$$

- Replace  $d^m y/dt^m$  with  $s^m Y(s)$ :

$$\left( s^n + a_1 s^{n-1} + a_2 s^{n-2} + \dots + a_{n-1} s + a_n \right) Y(s) =$$
$$\left( b_1 s^{n-1} + b_2 s^{n-2} + \dots + b_{n-1} s + b_n \right) U(s)$$

- Solving for  $Y(s)$  in terms of  $U(s)$  yields the transfer function as a ratio of polynomials:

$$Y(s) = H(s)U(s), \quad H(s) = \frac{N(s)}{D(s)}$$

$$N(s) = b_1 s^{n-1} + b_2 s^{n-2} + \dots + b_{n-1} s + b_n$$

$$D(s) = s^n + a_1 s^{n-1} + a_2 s^{n-2} + \dots + a_{n-1} s + a_n$$

- The transfer function governs the response of the output to the input with all initial conditions set to zero.


# Combining Transfer Functions

- There are (easily derivable) rules for combining transfer functions


- Series: a series combination of transfer functions




reduces to

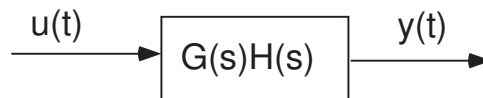

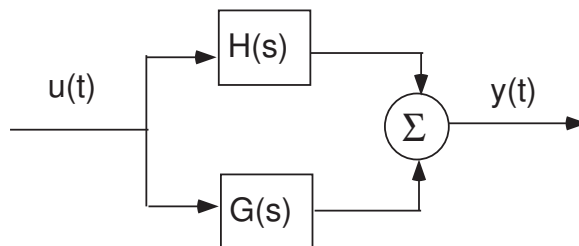- Parallel: a parallel combination of transfer functions




reduces to

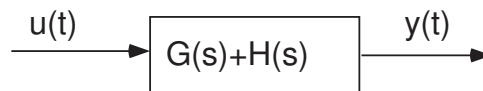


# Feedback Connection


- Consider the feedback system

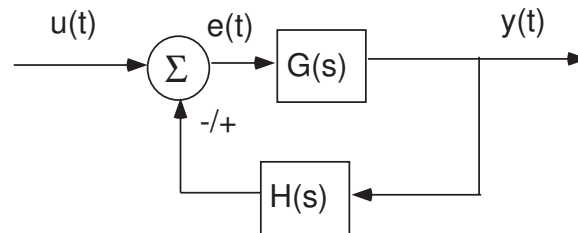

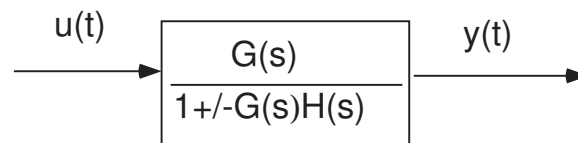- Feedback equations*: the output depends on the error, which in turn depends upon the output!
  - $y = Ge$
  - $e = u \mp Hy$
- If we use “negative feedback”, and  $H = 1$ , then  $e = y - u$ 
  - the input signal  $u$  is a “command” to the output signal  $y$
  - $e$  is the error between the command and the output
- Substituting (b) into (a) and solving for  $y$  yields



- The *error signal* satisfies

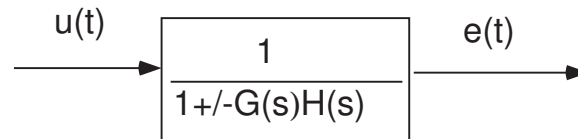

# Motor Transfer Functions, I

- Four different equations that govern motor response, and their transfer functions

- Current: Kirchoff's Laws imply

$$L \frac{dI}{dt} + RI = V - V_B$$

$$I(s) = \left( \frac{1}{sL + R} \right) (V(s) - V_B(s)) \quad (1)$$

- Speed: Newton's Laws imply

$$J \frac{d\Omega}{dt} = T_M - B\Omega - T_L$$

$$\Omega(s) = \left( \frac{1}{sJ + B} \right) (T_M(s) - T_L(s)) \quad (2)$$

- Torque:

$$T_M(s) = K_M I(s) \quad (3)$$

- Back EMF:


$$V_B(s) = K_V \Omega(s) \quad (4)$$

⇒ We can solve for the outputs  $T_M(s)$  and  $\Omega(s)$  in terms of the inputs  $V(s)$  and  $T_L(s)$



## Motor Transfer Functions, II

- Combine (1)-(4):

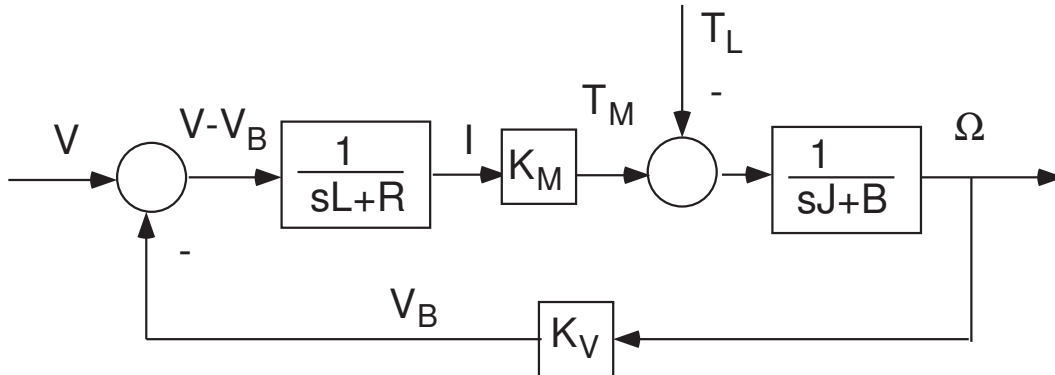


- Linear systems theory  $\Rightarrow$  the superposition principle holds  $\Rightarrow$  the response of  $\Omega$  to  $V$  and  $T_L$  is equal to the *sum* of the response to  $V$  and the response to  $T_L$ .
- Transfer function from Voltage to Speed (set  $T_L = 0$ ):
  - First combine (1)-(3)

$$\Omega(s) = \frac{K_M}{(sJ + B)} \frac{1}{(sL + R)} (V(s) - V_B(s))$$

- Then substitute (4) and solve for  $\Omega(s)$  in terms of  $V(s)$ :

$$\Omega(s) = \left( \frac{\frac{K_M}{(sL + R)}}{1 + \frac{K_M K_V}{(sJ + B)} \frac{1}{(sL + R)}} \right) \frac{1}{(sJ + B)} V(s) \quad (*)$$

## Motor Transfer Functions, III

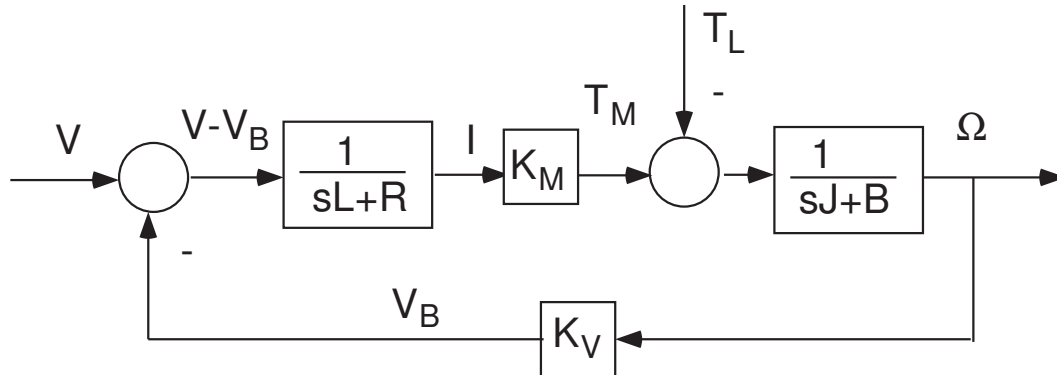

- Transfer function from Voltage to Motor Torque (set  $T_L = 0$ ):
  - First combine (1) and (3)

$$T_M(s) = \frac{K_M}{(sL + R)}(V(s) - V_B(s))$$

- Then substitute (4) and (2) and solve for  $T_M(s)$  in terms of  $V(s)$ :


$$T_M(s) = \left( \frac{\frac{K_M}{(sL+R)}}{1 + \frac{K_M K_V}{(sJ+B)} \frac{1}{(sL+R)}} \right) V(s) \quad (**)$$

- Comparing (\*) and (\*\*), we see that the speed response is equal to the torque response passed through a first order filter representing the mechanical motor dynamics.
- The steady state response of speed and torque to a constant voltage input  $V$  is obtained by setting  $s = 0$  (cf. Lecture 5):

$$\Omega_{ss} = \frac{K_M V}{RB + K_M K_V}, \quad T_{Mss} = \frac{K_M B V}{RB + K_M K_V}$$
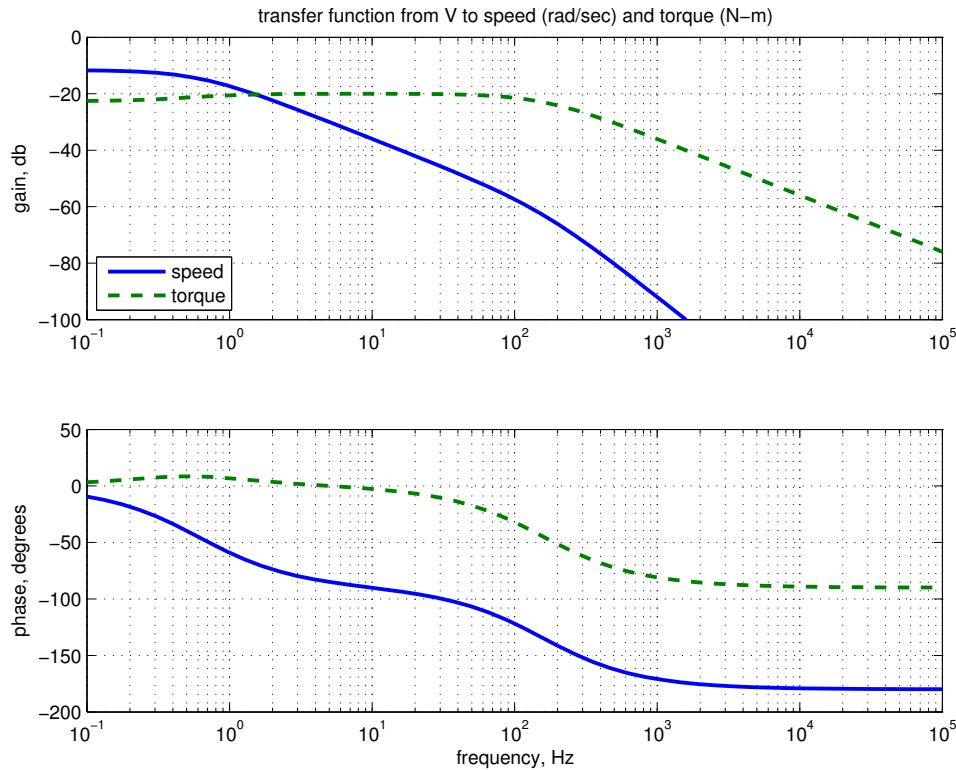
# Motor Frequency Response

- DC Motor is a lowpass filter<sup>2</sup>. Speed is filtered more than torque:



- Parameter Values

- $K_M = 1$  N-m/A
- $K_V = 1$  V/(rad/sec)
- $R = 10$  ohm
- $L = 0.01$  H
- $J = 0.1$  N-m/(rad/sec)<sup>2</sup>
- $B = 0.28$  N-m/(rad/sec)

- Why is frequency response important?


- Linear vs. PWM amplifiers . . .

---

<sup>2</sup>Matlab m-file DC\_motor\_freq\_response.m

# Linear Power Amplifier

- Voltage amplifiers:

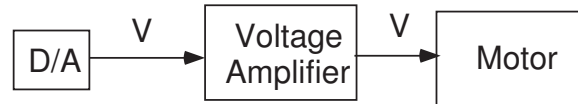

- output voltage is a scaled version of the input voltage, gain measured in  $V/V$ .
- Draws whatever current is necessary to maintain desired voltage
- Motor speed will depend on load:  $\Omega = \frac{K_M V - R T_L}{K_M K_V + R B}$

- Current (transconductance) amplifiers:




- output current is a scaled version of the input voltage, gain measured in  $A/V$ .
- Will produce whatever output voltage is necessary to maintain desired current
- Motor torque will not depend on load:  $T_M = K_M I$
- Advantage of linearity: Ideally, the output signal is a constant gain times the input signal, with no distortion
  - In reality, bandwidth is limited
  - Voltage and/or current saturation
- Disadvantage:
  - inefficient unless operating “full on”, hence tend to consume power and generate heat.

# Pulse Width Modulation


- Recall:
  - with no load, steady state motor speed is proportional to applied voltage
  - steady state motor torque is proportional to current (even with a load)
- With a D/A converter and linear amplifier, we regulate the level of applied voltage (or current) and thus regulate the speed (or torque) of the motor.
- PWM idea: Apply full scale voltage, but turn it on and off periodically
  - Speed (or torque) is (approximately) proportional to the average time that the voltage or current is on.
- PWM parameters:
  - switching period, seconds
  - switching frequency, Hz
  - duty cycle, %
- see the references plus the web page [2]

# PWM Examples


- 40% duty cycle<sup>3</sup>.

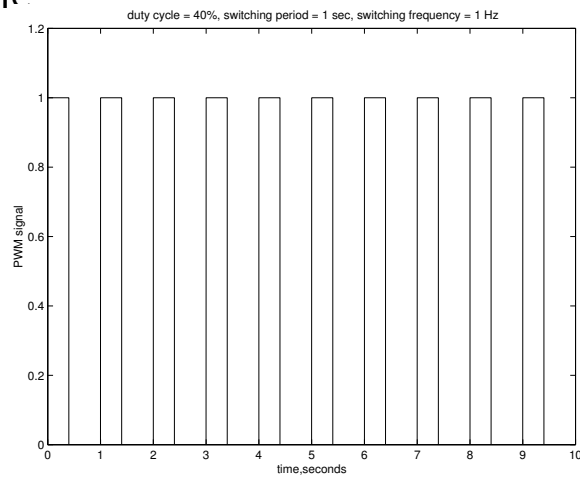

- 10% duty cycle.

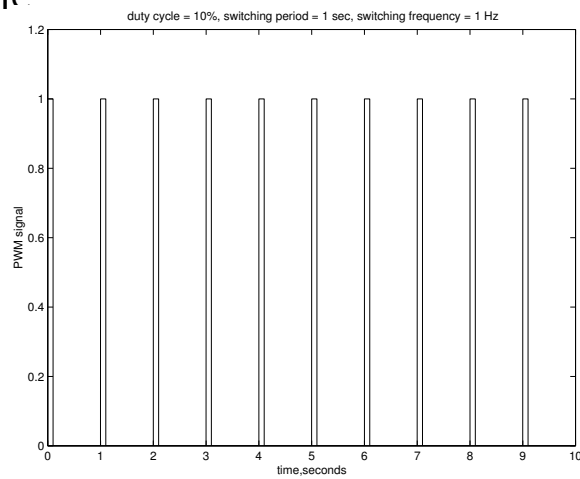


- 90% duty cycle.

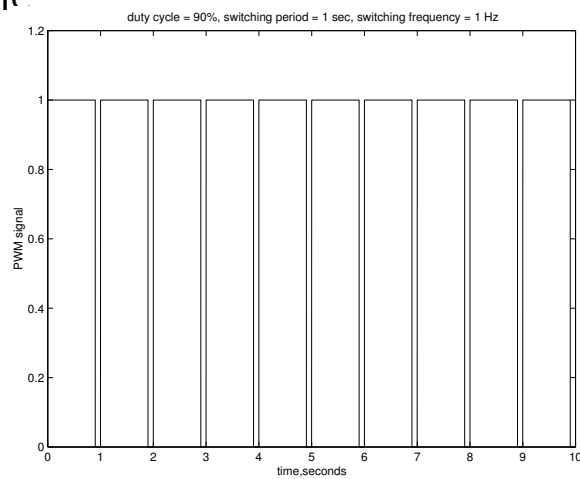


<sup>3</sup>Matlab files PWM\_plots.m and PWM.mdl
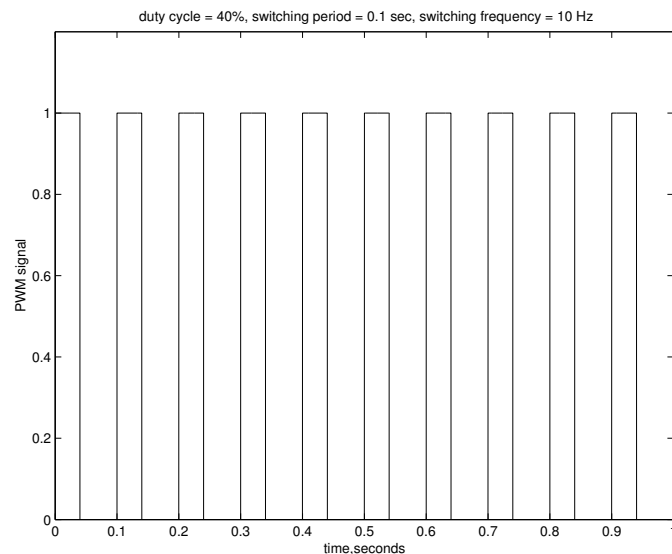
# PWM Frequency Response, I

- Frequency spectrum of a PWM signal will contain components at frequencies  $k/T$  Hz, where  $T$  is the switching period
- PWM input: switching frequency 10 Hz, duty cycle 40%<sup>4</sup>:



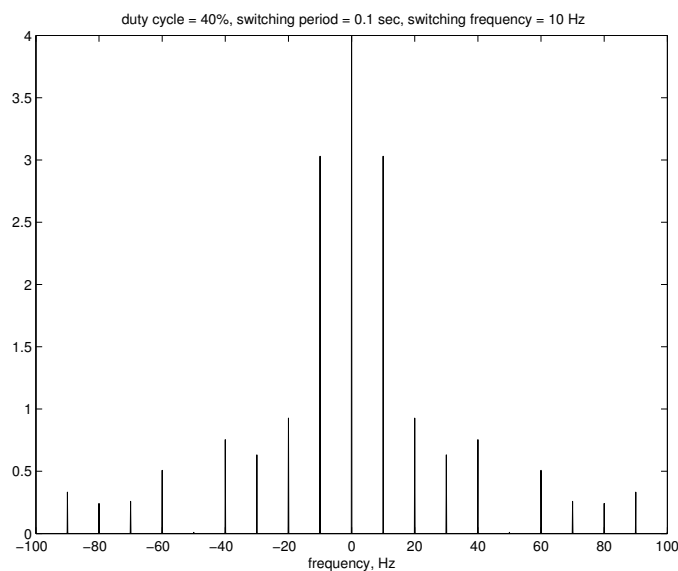- Frequency spectrum will contain
  - a nonzero DC component (because the average is nonzero)
  - components at multiples of 10 Hz




---


<sup>4</sup>Matlab files PWM\_spectrum.m and PWM.mdl
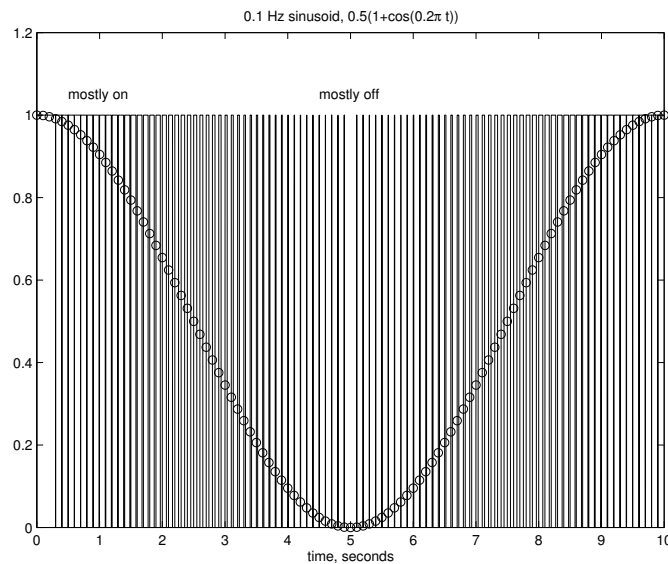
## PWM Frequency Response, II

- PWM signal with switching frequency 10 Hz, and duty cycle for the  $k$ 'th period equal to  $0.5(1 + \cos(.2\pi kT))$  (a 0.1 Hz cosine shifted to lie between 0 and 1, and evaluated at the switching times  $T = 0.1 \text{ sec}$ )<sup>5</sup>



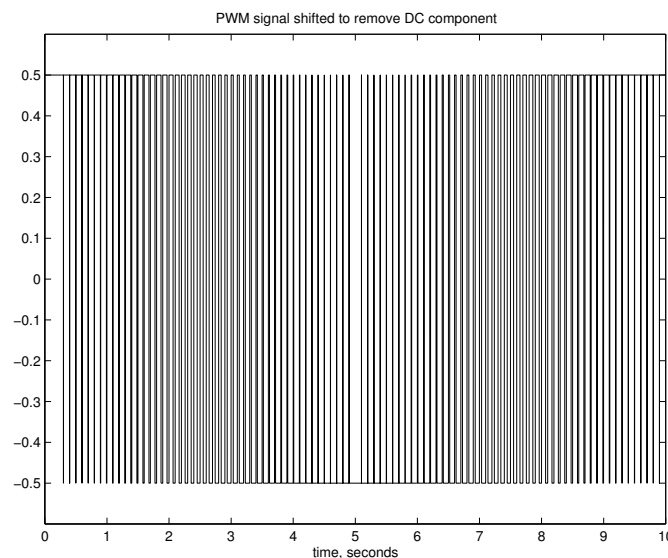- Remove the DC term by subtracting 0.5 from the PWM signal




<sup>5</sup>Matlab files PWM\_sinusoid.m and PWM.mdl


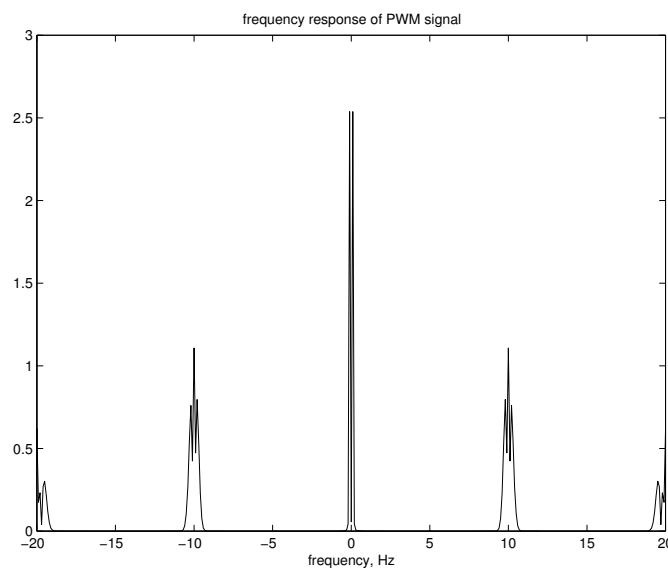
## PWM Frequency Response, III


- Frequency spectrum of PWM signal has
  - zero DC component
  - components at  $\pm 0.1$  Hz
  - components at multiples of the switching frequency, 10 Hz




- Potential problem with PWM control:
  - High frequencies in PWM signal may produce undesirable oscillations in the motor (or whatever device is driven by the amplified PWM signal)
  - switching frequency usually set  $\approx 25$  kHz so that switching is not audible
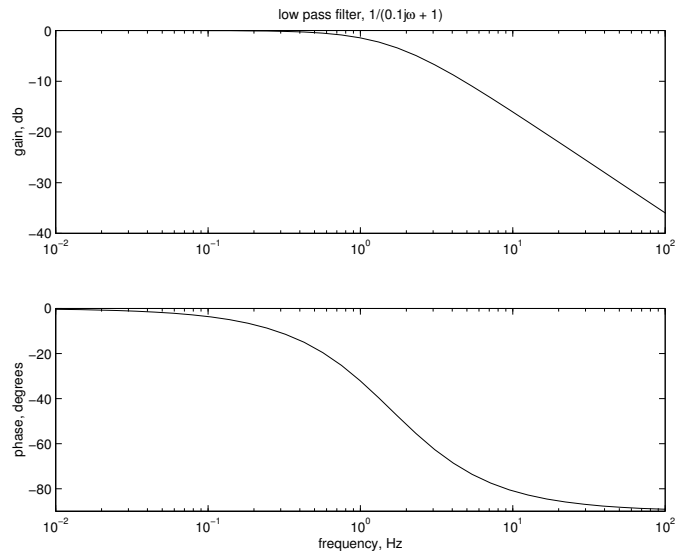
## PWM Frequency Response, IV

- Suppose we apply the PWM output to a lowpass filter that has unity gain at 0.1 Hz, and small gain at 10 Hz




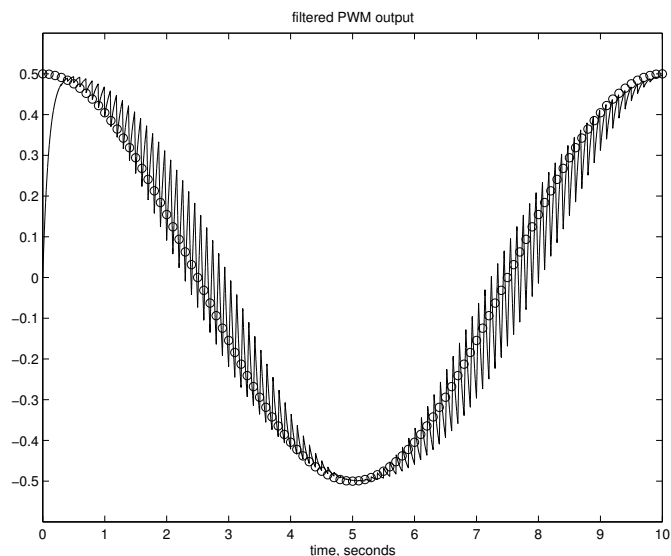- Then, after an initial transient, the filter output has a 0.1 Hz oscillation.



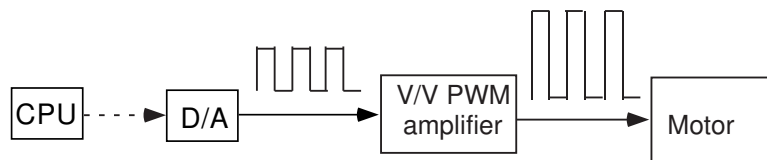
# PWM Generation

- Generate PWM using D/A and pass it through a PWM amplifier



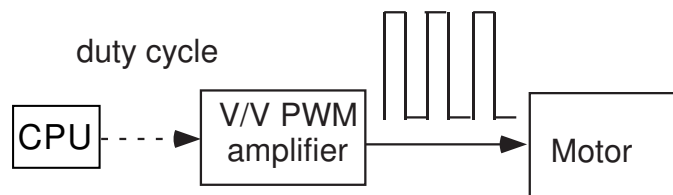- techniques for generating analog PWM output ([6]):
  - software
  - timers
  - special modules
- Feed the digital information directly to PWM amplifier, and thus bypass the D/A stage



- PWM voltage or current amplifiers
- must determine direction
  - normalize so that
    - \* 50% duty cycle represents 0
    - \* 100% duty cycle represents full scale
    - \* 0% duty cycle represents negative full scale
    - \* what we do in lab, plus we limit duty cycle to 35% – 65%
  - use full scale, but keep track of sign separately

## References

- [1] D. Auslander and C. J. Kempf. *Mechatronics: Mechanical Systems Interfacing*. Prentice-Hall, 1996.
- [2] M. Barr. Introduction to pulse width modulation. [www.oreillynet.com/pub/a/network/synd/2003/07/02/pwm.html](http://www.oreillynet.com/pub/a/network/synd/2003/07/02/pwm.html).
- [3] W. Bolton. *Mechatronics: Electronic Control Systems in Mechanical and Electrical Engineering, 2nd ed.* Longman, 1999.
- [4] C. W. deSilva. *Control Sensors and Actuators*. Prentice Hall, 1989.
- [5] G.F. Franklin, J.D. Powell, and A. Emami-Naeini. *Feedback Control of Dynamic Systems*. Addison-Wesley, Reading, MA, 3rd edition, 1994.
- [6] S. Heath. *Embedded Systems Design*. Newness, 1997.
- [7] C. T. Kilian. *Modern Control Technology: Components and Systems*. West Publishing Co., Minneapolis/St. Paul, 1996.
- [8] B. C. Kuo. *Automatic Control Systems*. Prentice-Hall, 7th edition, 1995.
- [9] J. B. Peatman. *Design with PIC Microcontrollers*. Prentice-Hall, 1998.